



# VIT<sup>®</sup>

Vellore Institute of Technology

(Deemed to be University under section 3 of UGC Act, 1956)

SCHOOL OF ELECTRICAL ENGINEERING

CAT - I

Fall Semester 2018 - 19

C<sub>1</sub> slot

Class Nbrs. : 0602, 0662 & 0645

Course Code : EEE 1001

Date of Exam : 14.08.2018

Course Title : Basic Electrical and Electronics Engineering

Max. Marks : 50


Faculty : R. M. Brisilla, R. Raja Singh, N. Arun

Duration : 1 ½ hours

Answer all the questions


1(a). Find  $I$  in the following circuit.

[5]

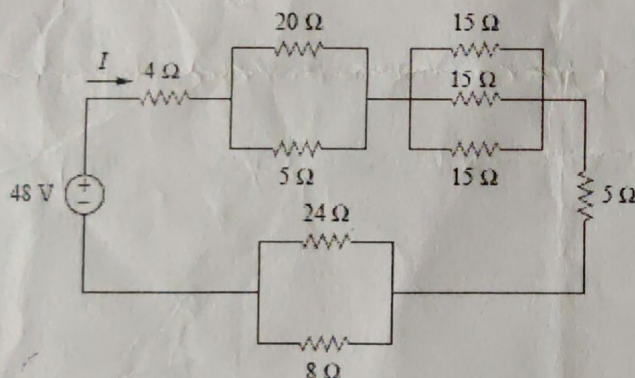

(b). Use source transformations to reduce the circuit in to a single voltage source in series with a single resistor.


[5]

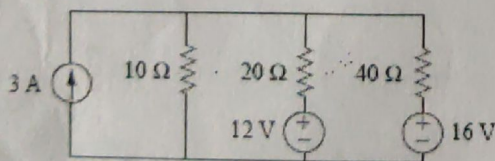

2. For the bridge network in Figure, find  $i_o$  and voltage across  $2k\Omega$  using mesh analysis


[10]



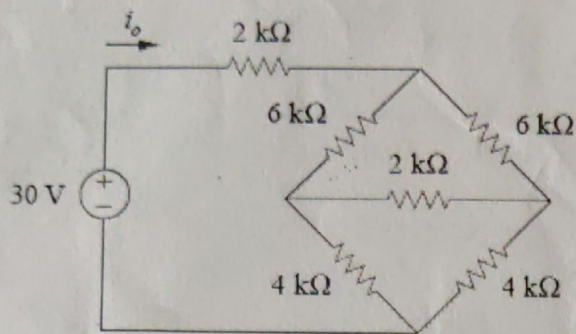


3. Using nodal analysis, find  $V_o$  in the circuit

[10]

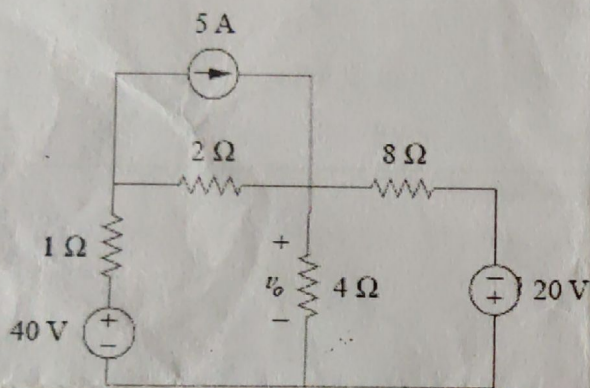

4. Apply Thevenin's theorem to find  $V_o$  in the following circuit.

[10]

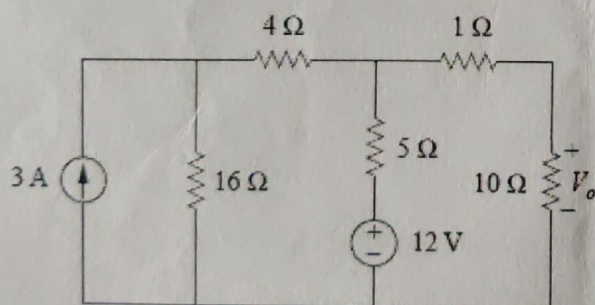

5. A coil of resistance  $5\Omega$  and inductance  $120\text{mH}$  in series with a  $100\mu\text{F}$  capacitor is connected to a  $300\text{V}$ ,  $50\text{Hz}$  supply. Calculate

[10]

- current flowing,
- phase difference between the supply voltage and current,
- voltage across the coil
- voltage across the capacitor.